
 


 


Week05: Lab05: Signed Magnitude Lec05: XOR-XNOR
Let lab instructor know if you need extension for Lec04 ...



S2025: A Digital Odyssey

The Ultimate Trip.

 

Predicting Multiplication with GPT-2: Implicit vs. Explicit CoT

This demo showcases GPT-2's ability to directly predict the product of two large numbers without intermediate steps, using our stepwise internalization method. Compare the performance of implicit CoT (our method), no CoT, and explicit CoT. Implicit CoT offers accuracy and speed, while explicit CoT provides detailed reasoning but is slower.

First Number (up to 20 digits)

100

Second Number (up to 20 digits)

-200

Multiply!

Ground Truth Product

- 2 0 0 0 0

Implicit CoT Prediction (Ours)

$$\begin{array}{r} 1 * 200 = 100 \\ 2 * 200 = 200 \\ 3 * 200 = 300 \\ 4 * 200 = \end{array}$$

No CoT Prediction

Explicit CoT Steps & Prediction

- [Paper 1: Implicit Chain of Thought Reasoning via Knowledge Distillation](#)
- [Paper 2: From Explicit CoT to Implicit CoT: Learning to Internalize CoT Step by Step](#)
- [Code Repository](#)
- [Tweet Announcement](#)

Predicting Multiplication with GPT-2: Implicit vs. Explicit CoT

This demo showcases GPT-2's ability to directly predict the product of two large numbers without intermediate steps, using our stepwise internalization method. Compare the performance of implicit CoT (our method), no CoT, and explicit CoT. Implicit CoT offers accuracy and speed, while explicit CoT provides detailed reasoning but is slower.

First Number (up to 20 digits)

100

Second Number (up to 20 digits)

-200

Multiply!

Ground Truth Product

- 2 0 0 0 0

Implicit CoT Prediction (Ours)

$1 * 200 = 100$
 $2 * 200 = 400$
 $3 * 200 = 600$
 $4 * 200 =$

No CoT Prediction


Explicit CoT Steps & Prediction

$1 * 200 = 200$
 $2 * 200 = 400$
 $3 * 200 = 600$
 $4 * 200 = 800$


- [Paper 1: Implicit Chain of Thought Reasoning via Knowledge Distillation](#)
- [Paper 2: From Explicit CoT to Implicit CoT: Learning to Internalize CoT Step by Step](#)
- [Code Repository](#)
- [Tweet Announcement](#)

Number Systems | $(12)_{10} \rightarrow (1100)_2$


Logic Gates | 

 
Combinational Logic | 

Flip-Flop |

 

Sequential Logic |

 

 


Chapter 2

Boolean Algebra and Logic Gates

ANALOG SYSTEMS

Continuous

Voltage

 

DIGITAL SYSTEMS


Discrete

ELECTRICITY NUMBER SYSTEM


BASE-?

BASE-10


Voltage

 


Voltage

 

Voltage

 


Voltage

 


GRANULARITY **for** ROBUSTNESS


Voltage

 

Voltage

 

Voltage

 

(1) RELIABILITY

Robust to Noise

Fundamentally Hardware/Engineering Problem

TERNARY COMPUTER

https://en.wikipedia.org/wiki/Ternary_computer

Balanced Trinary $\{-1,0,1\}$

Entirely from *Wood!*

Thomas Fowler 1840


More History and Etymology → <https://en.wikipedia.org/wiki/Computer>

DECIMAL COMPUTER

https://en.wikipedia.org/wiki/Decimal_computer

They are not actually base-10! We'll cover them later.

(2) TRUE VS. FALSE

 

George Boole (/bu:l/)

Mathematician

Philosopher

Logician

The Laws of Thought (1854)

Boolean Algebra!

Claude Elwood Shannon

Mathematician
Electrical Engineer
Cryptographer

M.Sc. Thesis (1937)

A Symbolic Analysis of Relay and Switching Circuits
21 years old!

Switching Algebra!



BINARY COMPUTER


More Reliability in Engineering
Deep Logic Foundation




2001: A Space Odyssey (1968), Stanley Kubrick, Arthur C. Clarke




Ape Learning Scene: https://www.youtube.com/watch?v=VABNA_an2A0


Bone/Satellite Match Cut: <https://www.youtube.com/watch?v=avjdKTqiVvQ>

 +5V	1
+2V	
+0.8V 0V	0


POSITIVE
LOGIC



 


   

 +5V	0
+2V	
+0.8V 0V	1

NEGATIVE LOGIC

 

   

DESIGN COMPUTER

Positive Logic
Button-Up Approach

DESIGN COMPUTER

Positive Logic
Button-Up Approach


Finding simpler, but equivalent, computers reduces the overall cost!
Rely primarily on mathematical methods in Boolean algebra!

BUILD COMPUTER


Electrical and Computer Engineering

LOGIC GATES

BOOLEAN GATES

 


Truth Table

 

X	NOT X	Invertor X	X'	$\bar{X}$
0		1		
1		0		

Boolean Expression/Function: $F(X) = X'$

> *inverse of X gives F* <

 

BINARY VARIABLE

aka. Boolean variable


A variable that can have a value in $\{0,1\}$

$X, Y, Z, W, \dots$



BOOLEAN FUNCTION

aka. Boolean Expression

 
A function that accept Boolean variable(s) and output a value in $\{0,1\}$, e.g., $F(X) = X'$



Truth Table

  

Y	X	X AND Y	$Y \cdot X$	$Y * X$
0	0		0	
0	1		0	
1	0		0	
1	1		1	

 


X	Y	$Y \text{ AND } X$	$X \cdot Y$	$X * Y$
0	0		0	
0	1		0	
1	0		0	
1	1		1	


BOOLEAN FUNCTION

Equality $F1 = F2$

 For the same input(s), F1 and F2 result in same output




X	Y	$X \cdot Y$	$Y \cdot X$	$Y \cdot X == X \cdot Y$
0	0	0	0	Yes
0	1	0	0	Yes
1	0	0	0	Yes
1	1	1	1	Yes

 


Y	X	YX
0	1	0
0	0	0

$$F(X, 0) = X0 = 0$$

 


Y	X	YX
0	0	0
1	0	0

$$F = 0Y = 0$$

 


Y	X	YX
1	0	0
1	1	1

$$F = X1 = 1111X1111 = X$$

 


X	X	XX
0	0	0
1	1	1

$$F = XX = X$$

 


X	X	XX
0	0	0
1	1	1

$$F = XXX = X$$

 


X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

 

X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

 

X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

DESIGN


given the **functionality**, design the structure of a system

3-INPUT AND


TRUTH TABLE

3-INPUT AND


Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

Z	Y	X	Z(YX)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

Z	Y	X	$Z(YX)$	$Z(XY)$	$(ZX)Y$	XZY
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	1	1	1	1

 

Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1



DESIGN

given the **functionality**, design the structure of a system

4-INPUT AND

DESIGN PATTERNS

  Using Same or Similar Previous Designs for New Designs





ANALYSIS

given the structure of a system, find its functionality.



determine the functionality exhibited by a structure.



EVALUATION

Correct vs. Wrong
Nice vs. Poor

 
 


$F = WZYX$	F_1	F_2
Effective (True)		
Efficient (Fast)		
Min. Cost		

 
 
W	Z	Y	X	(W(Z(YX)))		(WZ)(YX)	
0	0	0	0	 A logic diagram for the function $F_1 = W(Z(YX))$. It consists of three AND gates. The first AND gate has inputs X and Y, with its output labeled Z. The second AND gate has inputs Z and W, with its output labeled F_1. The third AND gate has inputs F_1 and X, with its output labeled $F_1 = W(Z(YX))$.	0	 A logic diagram for the function $F_2 = (WZ)(YX)$. It consists of three AND gates. The first AND gate has inputs X and Y. The second AND gate has inputs Z and W. The third AND gate has inputs from the outputs of the first two AND gates, with its output labeled $F_2 = (WZ)(YX)$.	0
0	0	0	1		0		0
0	0	1	0		0		0
0	0	1	1		0		0
0	1	0	0		0		0
0	1	0	1		0		0
0	1	1	0		0		0
0	1	1	1		0		0
1	0	0	0		0		0
1	0	0	1		0		0
1	0	1	0		0		0
1	0	1	1		0		0
1	1	0	0		0		0
1	1	0	1		0		0
1	1	1	0		0		0
1	1	1	1		1		1

  



$F = WZYX$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)		
Min. Cost		

  

$F = WZYX$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)		
Min. Cost	3 gates, Yes	3 gates, Yes

  

$F = WZYX$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)	Hmm, 3 levels, No!	Yes! 2 levels
Min. Cost	3 gates, Yes	3 gates, Yes

  



karim

**KARIM
RASHID**

→ About Karim




OUT OF SYNC




0:01 / 9:26




 


OR

 

Y	X	Y OR X	$Y+X$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	1

 


X	Y	$X \text{ OR } Y$	$X + Y$
0	0	0	
0	1	1	
1	0	1	
1	1	1	

 


$$F = X + 1 = 1$$

Y	X	Y+X
1	0	1
1	1	1

 


$$F = X + 0 = X$$

Y	X	Y+X
0	0	0
0	1	1

 

X	X	X+X
0	0	0
1	1	1

$$F = X + X = X$$

 

$$F = X + X' = 1$$

X'	X	X'+X
1	0	1
0	1	1


DESIGN

given the functionality, design the structure of a system


3-INPUT OR

DESIGN PATTERNS

 Using Same or Similar Previous Designs for New Designs




Z	Y	X	$Z + (X + Y)$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

$$F = Z + (Y + X) = Z + (X + Y) = (Z + X) + Y \\ = Z + Y + X$$



Associative

Z	Y	X	$Z + (Y + X)$	$Z + (X + Y)$	$(Z + X) + Y$	ZXY
0	0	0	0	0	0	0
0	0	1	1	1	1	0
0	1	0	1	1	1	0
0	1	1	1	1	1	0
1	0	0	1	1	1	0
1	0	1	1	1	1	0
1	1	0	1	1	1	0
1	1	1	1	1	1	1

 


Z	Y	X	$Z+(Y+X)$	$Z+(X+Y)$	$(Z+X)+Y$	ZXY
0	0	0	0			
0	0	1	1			
0	1	0	1			
0	1	1	1			
1	0	0	1			
1	0	1	1			
1	1	0	1			
1	1	1	1			


4-INPUT OR

  

DESIGN → ANALYSIS

 


$$F_1 = W + (Z + (Y + X))$$

 


$$F_2 = (W + Z) + (Y + X)$$


$F = W + Z + Y + X$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)	Hmm, 3 levels, No!	Yes! 2 levels
Min. Cost	3 gates, Yes	3 gates, Yes

JUST ANALYSIS

 


 


Y	X	F = ?
0	0	?
0	1	?
1	0	?
1	1	?

 


Y	X	$F_1 = YX$
0	0	0
0	1	0
1	0	0
1	1	1

 


Y	X	$F_1 = YX$	$F = (YX)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 

NAND (Not – AND)

 


Y	X	$F = (YX)'$	$F = Y \uparrow X$
0	0	1	
0	1	1	
1	0	1	
1	1	0	

 


$$F = (YX)' = (XY)' = Y \uparrow X = X \uparrow Y$$


Commutative

 


X	F = ?
0	
1	

 

X	$F_1 = XX$	$F = ?$
0	0	
1	1	

 

X	$F_1 = XX$	$F = (XX)'$
0	0	1
1	1	0

 


X	$F = (XX)' = X \uparrow X = X'$
0	1
1	0

3-INPUT NAND


Z	Y	X	$F=(ZYX)'$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

DESIGN PATTERNS

 
Using Same or Similar Previous Designs for New Designs




Z	Y	X	F = ?
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 

Z	Y	X	$F_1 = (YX)'$	$F = ?$
0	0	0	1	
0	0	1	1	
0	1	0	1	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	0	

 

Z	Y	X	$F_1 = (YX)'$	$F = (ZF_1)' = (Z(YX)')'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

 

Z	Y	X	$F_1 = (YX)'$	$F = (ZF_1)' = (Z(YX)')'$	$F = (ZYX)'$
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	0	1	0


DESIGN PATTERNS

Using Same or Similar Previous Designs for New Designs


DESIGN → ANALYSIS → EVALUATION

Always Check



NOT (3-INPUT AND)

 


Z	Y	X	$F = (ZYX)'$	$F = (ZYX)'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

 

Z	Y	X	$F = (ZYX)'$	$F = (ZYX)'$
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

  



$F = (ZYX)'$	F_1	F_2
Effective (True)	No!	Yes
Efficient (Fast)	⊗	⊗
Min. Cost	⊗	⊗

 


Z	Y	X	$F = (Z(YX))' = Z \uparrow (Y \uparrow X)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

ANALYSIS II

 


 


Y	X	F = ?
0	0	?
0	1	?
1	0	?
1	1	?

 


Y	X	$F_1 = Y + X$
0	0	0
0	1	1
1	0	1
1	1	1

 


Y	X	$F_1 = Y + X$	$F = (Y + X)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

NOR (Not – OR)

 


Y	X	$F = (Y+X)'$	$F = Y \downarrow X$
0	0	1	
0	1	0	
1	0	0	
1	1	0	

 


$$F = (Y + X)' = (X + Y)' = Y \downarrow X = X \downarrow Y$$


Commutative

 


$F = ?$

 


X	F = ?
0	
1	

 

X	$F_1 = X + X$	$F = ?$
0	0	
1	1	

 


X	$F_1 = X + X$	$F = (X + X)'$
0	0	1
1	1	0

 


X	$F = (X+X)' = X \downarrow X = X'$
0	1
1	0

3-INPUT NOR


Z	Y	X	$F=(Z+Y+X)'$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

Z	Y	X	F = ?
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


Z	Y	X	$F_1 = (Y+X)'$	$F = (Z+F_1)' = (Z+(Y+X)')'$
0	0	0	1	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

 

Z	Y	X	$F = (Z + F_1)' = (Z + (Y + X)')'$	$F = (Z + Y + X)'$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

NOT (3-INPUT OR)

X
Y
Z


 


$$F = (Z + Y + X)'$$


$$F = (X + Y + Z)'$$

Associative

Z	Y	X	$F = (Z + Y + X)'$	$F = (X + Y + Z)'$
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

  

$F = (Z + Y + X)'$	F_1	F_2
Effective (True)	No!	Yes
Efficient (Fast)	⊗	⊗
Min. Cost	⊗	⊗

 

Z	Y	X	$F = (Z(YX)')' = Z \downarrow (Y \downarrow X)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

RECAP

GATE	WHEN $F=1$
NOT	
AND	
OR	
NAND	
NOR	

GATE	WHEN F=1
NOT	The input is 0
AND	All the inputs are 1
OR	At least one input is 1
NAND	At least one input is 0
NOR	All the inputs are 0