

A deep-field astronomical image showing a vast field of galaxies in various colors (blue, orange, white) against a black background. Two horizontal blue lines are positioned above and below the central text.

Informal Survey on Course Delivery

<https://forms.gle/PxEKCHUv69XU45478>

<https://www.mouser.ca/c/semiconductors/logic-ics/logic-gates/>

Applied Filters: Semiconductors Logic ICs **Logic Gates** ✕

[Reset All](#)
[Apply Filters](#)

Search within results

Part # / Keyword 

- ☐ In Stock ☐ Active ☐ RoHS Compliant
☐ Normally Stocked ☐ New Products


Buy Selected

Compare Selected (up to 20)


Download Table (.CSV)

Select	Image	Part #	Mfr.	Description	Datasheet	Availability	Pricing (CAD)	Qty.	RoHS	ECAD Model	Logic	Number	Logic	Number	Pack
--------	-------	--------	------	-------------	-----------	--------------	---------------	------	------	------------	-------	--------	-------	--------	------


Number Systems | $(12)_{10} \rightarrow (1100)_2$
Logic Gates |

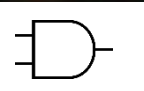


Combinational Logic |

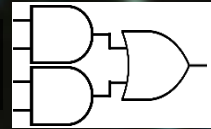

Flip-Flop |

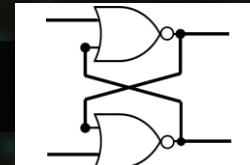


Sequential Logic |

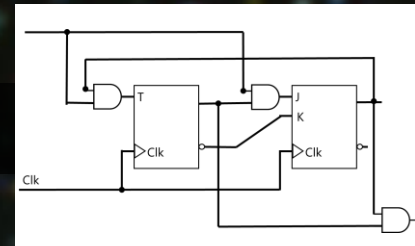


RECAP

Any Boolean Function F:

- Sum (OR) of Products (ANDs)
- Sum of **minterms** for Entries with **1**
 - ANDs-OR
 - NAND via $(F')'$
- Product (AND) of Sums (ORs)
- Product of **MAXTERMS (NOT minterms)** for Entries with **0**
 - ORs-AND
 - NOR via $(F')'$

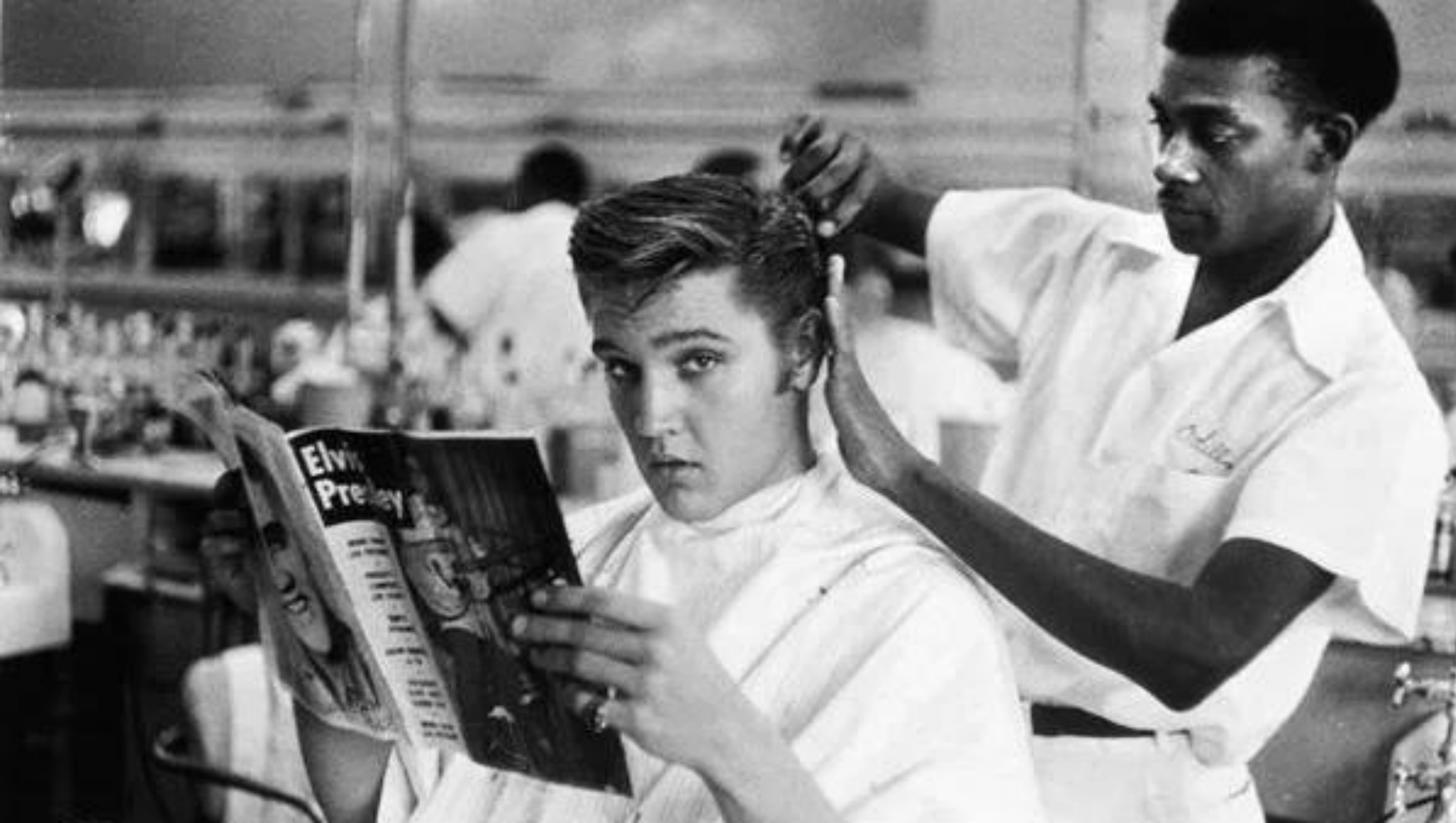

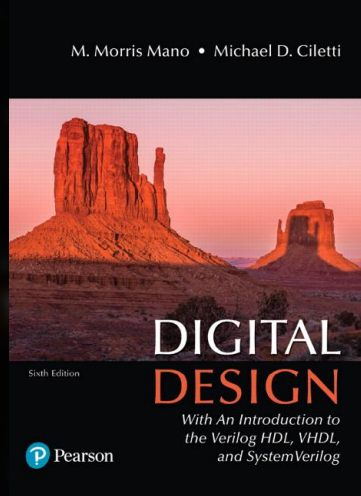

Chapter 2: Boolean Algebra and Logic Gates

Chapter 3: Gate-Level Minimization

MINIMIZATION

aka. Simplification

Same Effective Design but More Efficient

MINIMIZATION

Number of Gates

Number of Inputs (2-input vs 4-input)

Number of Interconnections

Propagation Time

Cost of Gates

Circuit Area

...

A circuit may not satisfy all due to conflicting constraints!

MINIMIZATION

aka. Simplification

SoP (ANDs-OR) → Simplify → NAND
PoS (ORs-AND) → Simplify → NOR

MINIMIZATION

- I) Boolean Algebra (algebraically)
 - II) Map (Karnaugh map, K-map)
-

MINIMIZATION


- I) Boolean Algebra (algebraically)
 - II) Map (Karnaugh map, K-map)
-

ALGEBRA

A set of elements

A set of operators

A set of axioms | postulates | assumptions | definitions

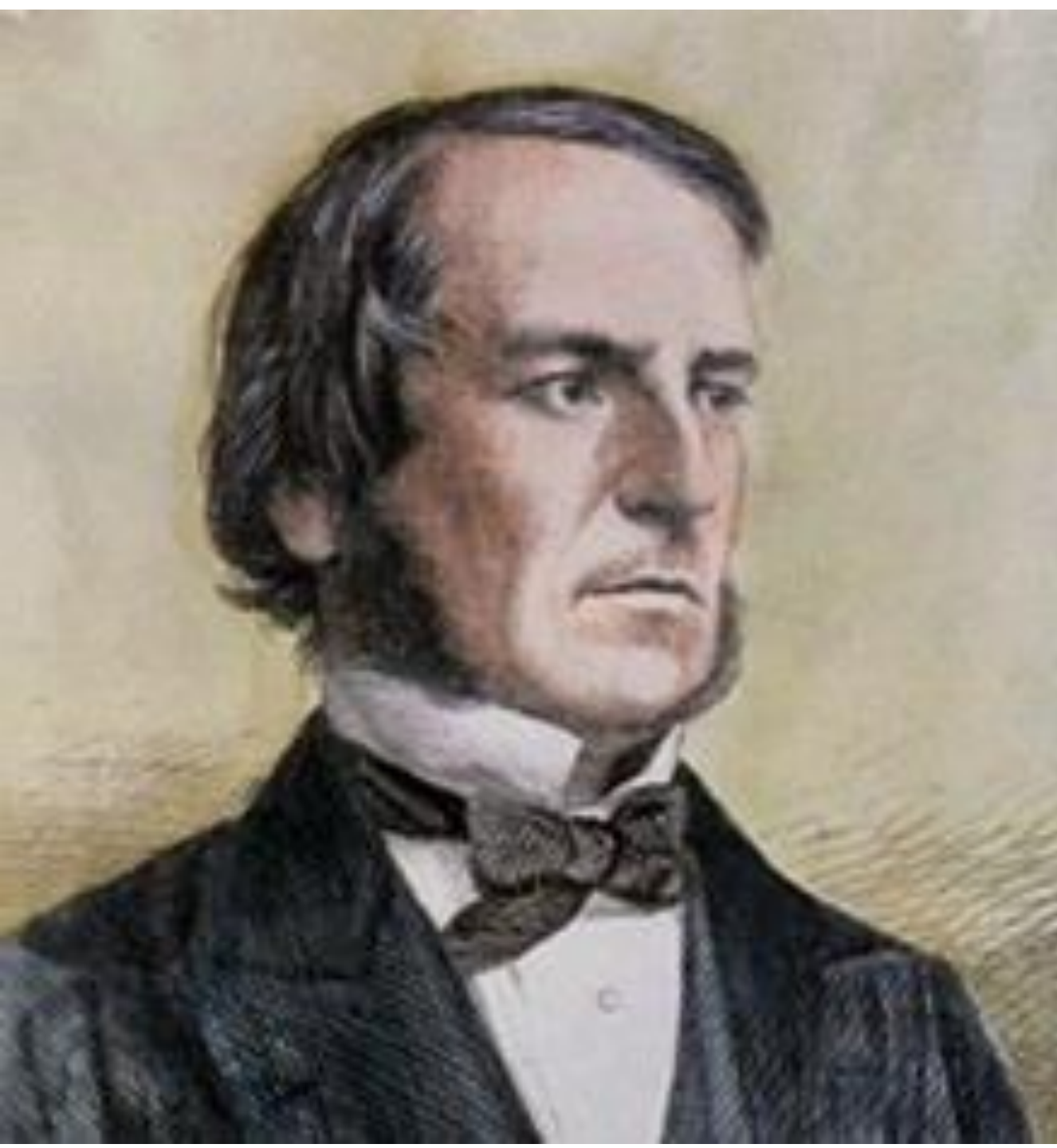

George Boole (/bu:l/)

Mathematician

Philosopher

Logician

The Laws of Thought (1854)

Boolean Algebra!



Edward Vermilye Huntington
1874 – 1952

In 1904, he put Boolean algebra
on a sound axiomatic foundation

POSTULATE

aka. Axiom, Assumption

<https://en.wikipedia.org/wiki/Axiom>

A statement that is **taken** to be **TRUE**

Serve as a premise or starting point for further reasoning

Section Sign --> Elvis, Just a Random Operator



I. CLOSURE

A set is closed with respect to an operator $\S$ iff the result of $\S \in S$:

Unary: $x \in S: \S x \in S$

Binary: $x, y \in S: x \S y \in S$

if and only if



II. COMMUTATIVE

A binary operator $\S$ on a set S is commutative iff for all $x, y \in S$:

$$x \S y = y \S x$$

($x \S y$ may or may not be in S)

III. ASSOCIATIVE

A binary operator $\S$ on a set S is associative iff for all $x, y, z \in S$:

$$x \S (y \S z) = (x \S y) \S z = x \S y \S z$$

Intuitively, when you don't need parenthesis to indicate the order!

Dagger Sign --> Just Another Random Operator



IV. DISTRIBUTIVE

If $\S$ and $\dagger$ are two binary operators on a set S , $\S$ is distributive over $\dagger$ iff:

Left Distributivity: $x \S (y \dagger z) = (x \S y) \dagger (x \S z)$

Right Distributivity: $(y \dagger z) \S x = (y \S x) \dagger (z \S x)$

IV. DISTRIBUTIVE


If $\S$ and $+$ are two binary operators on a set S , $\S$ is distributive over $+$ iff:

$$\text{If } \S \text{ Commutative: } x \S (y + z) = (x \S y) + (x \S z) = (y + z) \S x$$



<https://www.yuvalrob.com/>

yuvalrob

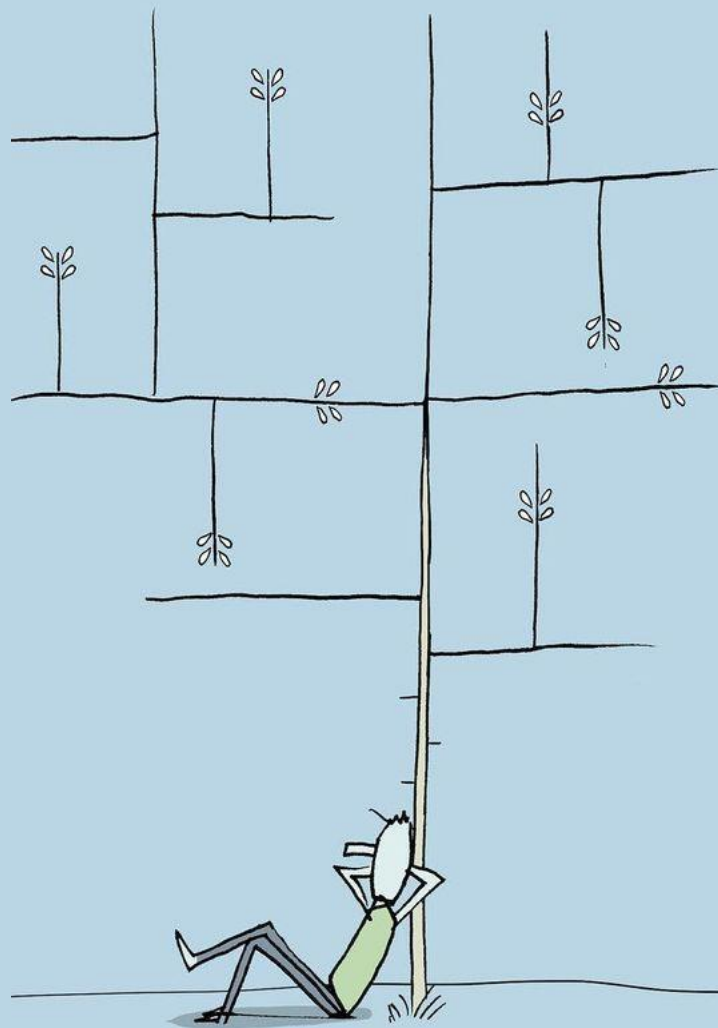

V. IDENTITY

$e \in S$ is an identity element w.r.t binary operator $\S$ iff for all $x \in S$:

$$x \S e = x = e \S x$$

VI. INVERSE



humans were originally created with four arms, four legs and a head with two faces. Fearing their power, Zeus split them into two separate parts, condemning them to spend their lives in search of their other halves.

VI. INVERSE

For all $x \in S$, there should be $y \in S$ w.r.t binary operator $\S$ iff:

$$x \S y = e_{\S} = y \S x$$

We denote $y = x^{-1}$ and $x = y^{-1}$

A painting of a woman with a needle in her chest. The woman is depicted from the chest up, with her eyes closed and a serene expression. She has a needle inserted into her upper chest, with a small amount of blood visible. Her right hand is raised, holding the needle. The background is a deep blue with intricate golden spiral patterns. The overall style is reminiscent of modernist or expressionist art.

Healing. -- Zara Mandana Fard
<https://www.baraneh.com/#/when-i-lost-hope/>

VII. COMPLEMENT

For all $x \in S$, there should be $y \in S$ w.r.t binary operators $\S$ and $\dagger$ iff:

$$x \S y = e_{\dagger} = y \S x$$

$$x \dagger y = e_{\S} = y \dagger x$$

We denote $y = x'$ and $x = y'$

VII. COMPLEMENT (NOT)

$$S = \{0,1\}$$

$$\S = + \text{ (OR)}, \times \text{ (AND)}$$

$$1+0=0+1 = e_{\times} = 1$$

$$0\times 1=1\times 0 = e_{+} = 0$$

$$0' = 1, 1' = 0$$

BOOLEAN ALGEBRA

- A set S with at least two elements x, y and $x \neq y$.
- Two binary operators $\&$ and $+$
- S is closed, commutative, distributive, and complement w.r.t $\&$, $+$
- $e_{\&}$ and e_{+} exist

Claude Elwood Shannon

Mathematician
Electrical Engineer
Cryptographer

M.Sc. Thesis (1937)

A Symbolic Analysis of Relay and Switching Circuits

Switching Algebra!

2-valued Boolean algebra



SWITCHING ALGEBRA

- $S = \{0, 1\}$
- $\cdot = \times$ (AND), $+$ (OR)
- S is closed, commutative, distributive, complement w.r.t $\times$, $+$
- $e_{\times} = 1$ and $e_{+} = 0$



$$0 \times 1 = e_{+} = 0$$

$$0 + 1 = e_{\times} = 1$$

$$0' = 1; 1' = 0$$

SWITCHING ALGEBRA IS-A BOOLEAN ALGEBRA

It satisfies all conditions of Boolean algebra!

Prove → Book: 2.3 axiomatic definition of Boolean algebra

Another sample of algebra in CS: Relational Algebra (SQL)

Is relational algebra a Boolean algebra? Check this when you take
COMP-3150: Database Management Systems!

[in]EQUALITY PROOF

Design A $\stackrel{?}{=}$ Design B

If $A \neq B$, Pick the Effective Design

If $A = B$, Pick the Efficient Design

[in]EQUALITY PROOF

prove by truth table

For equality proof, $F_1 = F_2$, for all possibility in the input variables (all rows), both side of equation must have equal value for same input variables.

For inequality proof, $F_1 \neq F_2$, find at least one possibility (a row) that have different values.

[in]EQUALITY PROOF

Prove by postulates

BASIC THEOREMS

Prove by postulates

OR gates   No Gate

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \\ &= (X + X) (X + X') \text{ using complement property} \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \\ &= (X + X) (X + X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x=1 \\ &= (X + X) (X+X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \\ &= X + 0 \text{ using complement property} \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x=1 \\ &= (X + X) (X+X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \\ &= X + 0 \text{ using complement property} \\ &= X \text{ using identity property of } e_+=0 \end{aligned}$$

OR gates   No Gate

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \\ &= X + X' \text{ using identity } e_x = 1 \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x=1 \\ &= (X + 1) (X+X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \\ &= X + X' \text{ using identity } e_x=1 \\ &= 1 \text{ using complement property} \end{aligned}$$

OR AND gates $\longleftarrow$ $\longrightarrow$ No Gates

$$X + XY = X$$

$$X + XY + XZW + \dots + XWAD = X$$

Absorption

$$X + XY = X$$

$$X + XY + XZW + \dots + XWAD = X$$

$X + XY =$
= $X1 + XY$ using identity $e_x = 1$
= $X(1 + Y)$ using distributive property of $\times$ over $+$
= $X1$ using previous theorem $x + 1 = 1$
= X using identity $e_x = 1$



Absorption

MINIMIZATION

- I) Boolean Algebra (algebraically)
aka. Algebraic Manipulation
-

EXAMPLE I

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND

1 × 4-input-OR

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

$$F = Z(Y'X' + YX + YX' + Y'X)$$

$$F = Z(Y'X' + YX + YX' + Y'X)$$

$$F = Z(Y'(X' + X) + YX + YX')$$

$$F = Z(Y'(X' + X) + YX + YX')$$

$$F \equiv Z(Y'1 + YX + YX')$$

$$F \equiv Z(Y'1 + YX + YX')$$

$$F \equiv Z(Y' + YX + YX')$$

$$F \equiv Z(Y' + YX + YX')$$

$$F \equiv Z(Y' + Y(X + X'))$$

$$F \equiv Z(Y' + Y(X + X'))$$

$$F = Z(Y' + Y1)$$

$$F = Z(Y' + Y)$$

$$F = Z(Y' + Y)$$

$$F = Z1$$

$$F = Z$$

0 gates!

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND
1 × 4-input-OR

EXAMPLE I

Another Approach

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

$$F = ZY'(X' + X) + ZYX + ZYX'$$

$$F \equiv ZY' (X' + X) + ZYX + ZYX'$$

$$F \equiv ZY' (X' + X) + ZY (X + X')$$

$$F \equiv ZY' (X' + X) + ZY (X + X')$$

$$F = ZY'1 + ZY1$$

$$F \equiv ZY' + ZY$$

$$F = Z(Y' + Y)$$

$$F = Z1$$

$$F = Z$$

0 gates!


$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND
1 × 4-input-OR

EXAMPLE I

Another Approach

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

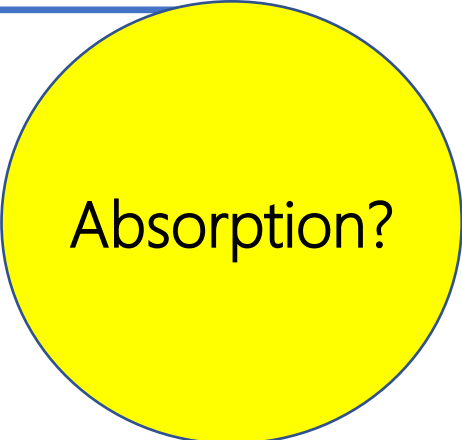

Absorption?

EXAMPLE II

$$F = ZY'X' + ZYX' + Z'Y'X$$

3 × 3-input-AND

1 × 3-input-OR

$$F = ZY'X' + ZYX' + Z'Y'X$$

$$F = ZX'(Y' + Y) + Z'Y'X$$

$$F = ZX' (Y' + Y) + Z'Y'X$$

$$F = ZX'1 + Z'Y'X$$

$$F = ZX' + Z'Y'X$$

1 × 2-input-AND

1 × 3-input-AND

1 × 2-input-OR

$$F = ZYX' + ZYX' + Z'Y'X$$

3 × 3-input-AND
1 × 3-input-OR

DUALITY THEORY

DUALITY

$\text{Dual}(F) = \text{OR} \Leftrightarrow \text{AND}, 1 \Leftrightarrow 0$

Dual(F) may or may not equal to F!

Be Careful! It's not the de Morgan law $(X+Y)' = X'Y'$

DUALITY

$$X+1 \Leftrightarrow X0$$

$$X+X' \Leftrightarrow XX'$$

$$(X+Y)' \Leftrightarrow (XY)'$$

DUALITY FOR COMPLEMENT (NOT)

DUALITY FOR COMPLEMENT (NOT)

$$F = A + (BC) \rightarrow F' = [A + (BC)]' = [A'(BC)'] = [A'(B' + C')]$$

DUALITY FOR COMPLEMENT (NOT)

$$F = A + (BC) \rightarrow \text{Dual}(F) \rightarrow A(B + C) \rightarrow F' = A'(B' + C')$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$

What's F' ?

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$

What's F' ?

$$F' = [AB(C + (DL'G(B' + A + E)))(H + (J'A'B))]'$$

$$F' = [AB(\dots)(H + (J'A'B))]'$$

$$F' = [A' + B' + (\dots)' + (H + (J'A'B))']$$

$$F' = [A' + B' + (\dots)' + (H'(J'A'B)')]$$

$$F' = [A' + B' + (\dots)' + (H'(J + A + B'))]$$

$$F' = [A' + B' + (C + (\dots))' + (H'(J + A + B'))] \text{ OMG!}$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A +$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A + B$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A + B + ($$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A + B + (C$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$


What's F' ?

$$\text{Dual}(F) = A + B + (C($$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$

What's F' ?

$$\text{Dual}(F) = A + B + (C(D + L' + G + (B'AE)))(H(J' + A' + B))$$

$$F = AB(C + (DL'G(B' + A + E)))(H + (J'A'B))$$

What's F' ?

$$\text{Dual}(F) = A + B + (C(D + L' + G + (B'AE)))(H(J' + A' + B))$$

Complement all variables only!

$$F' = A' + B' + (C'(D' + L + G' + (BA'E')))(H'(J + A + B'))$$

DUALITY THEOREM

A postulate or a proved theorem for F , also a postulate or a proved theorem for $\text{Dual}(F)$

DUALITY

$$\{X+1=1\} \Leftrightarrow \{X0 = 0\}$$

$$\{X+X'=1\} \Leftrightarrow \{XX'=0\}$$

$$\{(X+Y)'=X'Y'\} \Leftrightarrow \{(XY)'=X'+Y'\}$$

$$X(X + Y) = X$$

$$X(X + Y)(X + Z) \dots (X + W) = X$$

$\{X(X + Y) = X\} \rightleftharpoons \{X + XY = X\}$
 $\rightleftharpoons$ We proved the dual version
 $\rightleftharpoons$ Using the duality property, this is also true!



Absorption

DESIGN RECAP

SoP (ANDs-OR) $\rightarrow$ NAND

PoS (ORs-AND) $\rightarrow$ NOR

Given two unsigned numbers x and y , design a logic circuit to see

$$x \geq? y$$

What is the range of x and y ?

$$x \geq y$$

What is the range of x and y ?

$$x, y \in [0, 3]_{10}$$

What is the range of x and y ?

$$x, y \in [0, 3]_{10} = [00, 11]_2$$

What is the range of output?

$$F \in \{0, 1\}$$

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=?
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=Σ m(0,1,2,3,5,6,7,10,11,15)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=Π M(4,8,9,12,13,14)
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Y2	Y1	X2	X1	F(Y2,Y1,X2,X1)=Σ m(0,1,2,3,5,6,7,10,11,15)	F(Y2,Y1,X2,X1)=Π M(4,8,9,12,13,14)
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	1	1

Which design?

Which design?

SoP and PoS are both effective

SoP and PoS have same efficiency (2-levels)

Which design?


Cost: How many gates in SoP vs. PoS?

	$F(Y_2, Y_1, X_2, X_1) =$ $\Sigma m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) =$ $\Pi M(4, 8, 9, 12, 13, 14)$
AND	?	?
OR	?	?
NOT	?	?
NAND	?	?
NOR	?	?

	$F(Y_2, Y_1, X_2, X_1) = \sum m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
AND	Each minterm one 4-input-AND	Each MAXTERM one 4-input-OR
OR	One final 10-input-OR	One final 6-input-AND
NOT	Doesn't Matter Much	Doesn't Matter Much


	$F(Y_2, Y_1, X_2, X_1) = \sum m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
AND	10 $\times$ 4-input-AND	6 $\times$ 4-input-OR
OR	10-input-OR = 3 $\times$ 4-input-OR	6-input-AND = 2 $\times$ 4-input-AND
NOT	Doesn't Matter Much	Doesn't Matter Much

	$F(Y_2, Y_1, X_2, X_1) = \sum m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
AND	10 $\times$ 4-input-AND	6 $\times$ 4-input-OR
OR	10-input-OR = 3 $\times$ 4-input-OR	6-input-AND = 2 $\times$ 4-input-AND
NOT	Doesn't Matter Much	Doesn't Matter Much

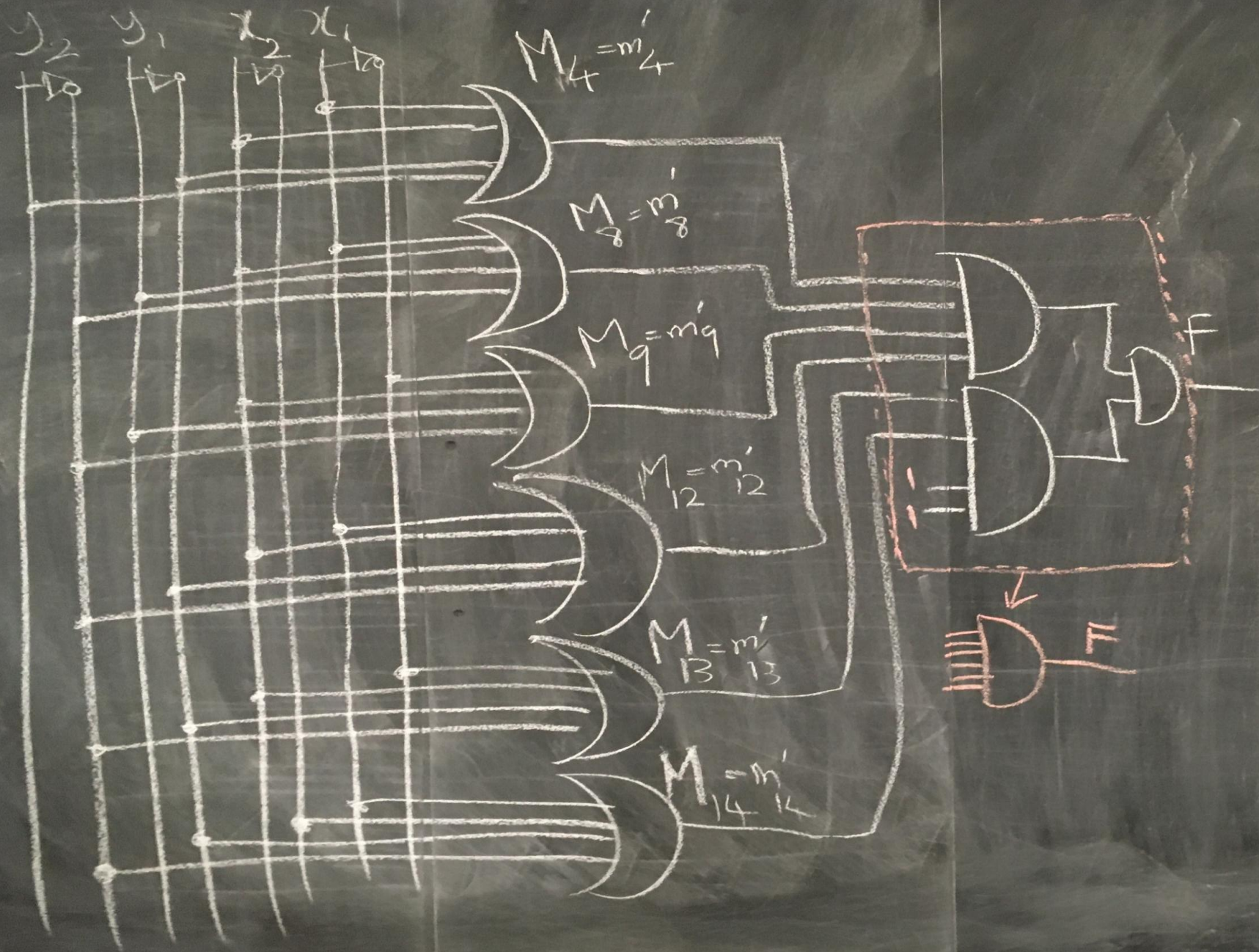

$$\begin{aligned}
 F &= \prod M(4, 8, 9, 12, 13, 14) \\
 &= M_4 M_8 M_9 M_{12} M_{13} M_{14} \\
 &= m'_4 m'_8 m'_9 m'_{12} m'_{13} m'_{14} \\
 &= (y'_2 y'_1 x'_2 x'_1) m'_4 \rightarrow y'_2 + y'_1 + x'_2 + x'_1 \\
 &\quad (y'_2 y'_1 x'_2 x'_1) m'_8 \rightarrow y'_2 + y'_1 + x'_2 + x'_1 \\
 &\quad (y'_2 y'_1 x'_2 x'_1) m'_9 \rightarrow y'_2 + y'_1 + x'_2 + x'_1 \\
 &\quad (y'_2 y'_1 x'_2 x'_1) m'_{12} \rightarrow y'_2 + y'_1 + x'_2 + x'_1 \\
 &\quad (y'_2 y'_1 x'_2 x'_1) m'_{13} \rightarrow y'_2 + y'_1 + x'_2 + x'_1 \\
 &\quad (y'_2 y'_1 x'_2 x'_1) m'_{14} \rightarrow y'_2 + y'_1 + x'_2 + x'_1
 \end{aligned}$$

	$F(Y_2, Y_1, X_2, X_1) = \sum m(0, 1, 2, 3, 5, 6, 7, 10, 11, 15)$	$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$
NAND	$10 \times 4\text{-input-NAND}$ $+$ $1 \times 10\text{-input-NAND}$	
NOR		$6 \times 4\text{-input-NOR}$ $+$ $1 \times 6\text{-input-NOR}$

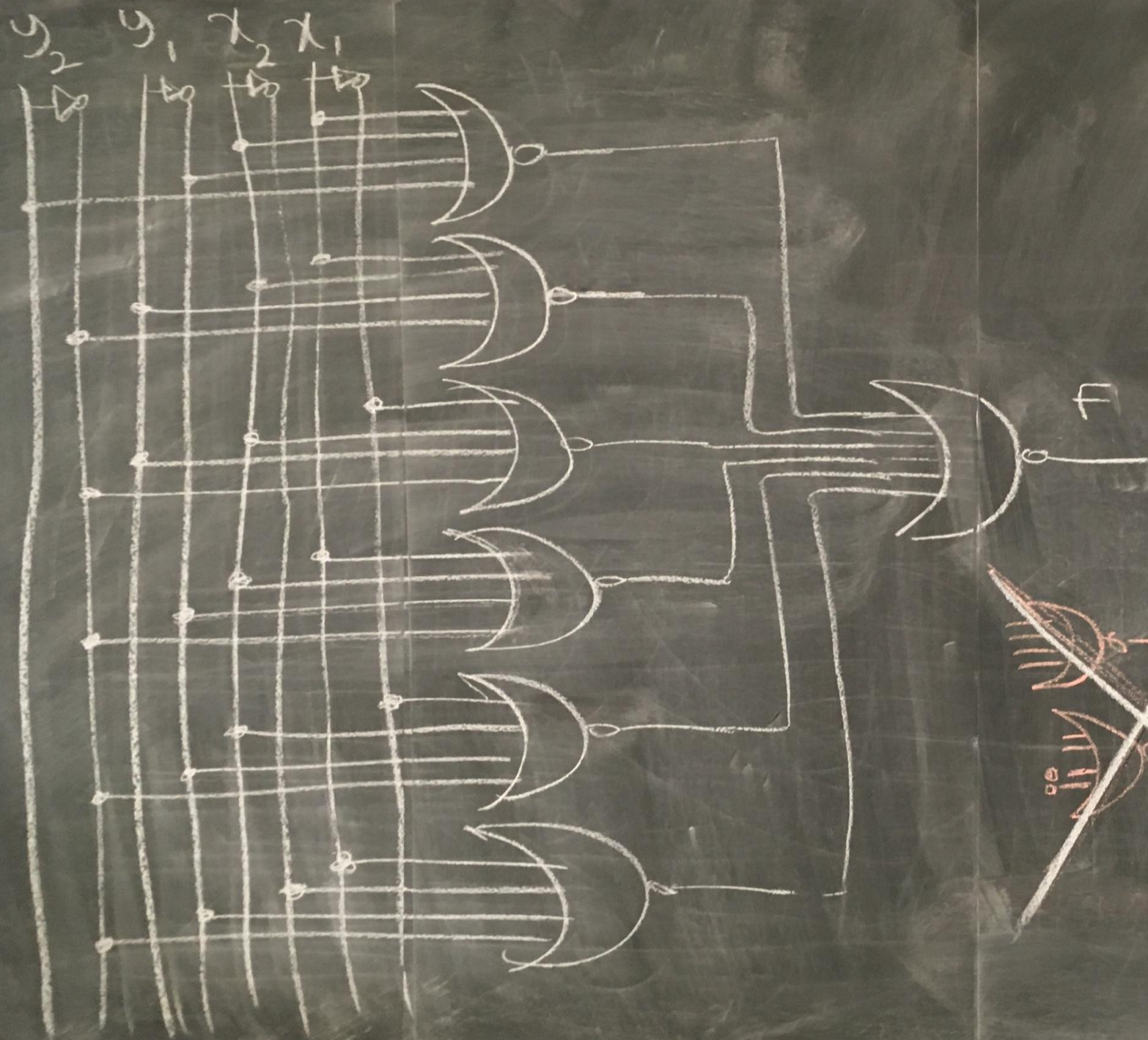

$$F = \prod M(4, 8, 9, 12, 13, 14)$$

$$= M_4 M_8 M_9 M_{12} M_{13} M_{14}$$

$$F = (F')'$$

$$= \left(M_4 M_8 M_9 M_{12} M_{13} M_{14} \right)'$$

$$= (M_4' + M_8' + M_9' + M_{12}' + M_{13}' + M_{14}')'$$

$$= (y_2 + y_1 + x_2 + x_1)'$$

$$+ (y_2' + y_1 + x_2 + x_1)'$$

$$+ (y_2' + y_1 + x_2 + x_1)'$$

$$+ (y_2' + y_1 + x_2 + x_1)'$$

$$+ (y_2' + y_1 + x_2 + x_1)'$$

$$+ (y_2' + y_1 + x_2 + x_1)'$$

$$\begin{aligned}
 F(Y_2, Y_1, X_2, X_1) &= \prod M(4, 8, 9, 12, 13, 14) \\
 &= (M4)(M8)(M9)(M12)(M13)(M14) \\
 &= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)
 \end{aligned}$$

OMG!!

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$\begin{aligned}
F(Y_2, Y_1, X_2, X_1) &= \prod M(4, 8, 9, 12, 13, 14) \\
&= (M4)(M8)(M9)(M12)(M13)(M14) \\
&= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1) \\
\text{Dual} &\rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)
\end{aligned}$$

Are we done?!

$$\begin{aligned}
F(Y_2, Y_1, X_2, X_1) &= \prod M(4, 8, 9, 12, 13, 14) \\
&= (M4)(M8)(M9)(M12)(M13)(M14) \\
&= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1) \\
\text{Dual} &\rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)
\end{aligned}$$

OMG!!

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)$$

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 (X'_1 + X_1)) + (Y'_2 Y'_1 X'_2 X_1)$$

$$\begin{aligned}
F(Y_2, Y_1, X_2, X_1) &= \prod M(4, 8, 9, 12, 13, 14) \\
&= (M4)(M8)(M9)(M12)(M13)(M14) \\
&= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1) \\
\text{Dual} &\rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y'_1 X_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 (X'_1 + X_1)) + (Y'_2 Y'_1 X'_2 X_1) \\
&= (Y_2 Y'_1 X_2 X_1) + (X_2 X_1 Y'_2) + (Y'_2 Y'_1 X_2 (1)) + (Y'_2 Y'_1 X'_2 X_1)
\end{aligned}$$

OMG!!

$$F(Y_2, Y_1, X_2, X_1) = \prod M(4, 8, 9, 12, 13, 14)$$

$$= (M4)(M8)(M9)(M12)(M13)(M14)$$

$$= (Y_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X_1)(Y'_2 + Y'_1 + X_2 + X'_1)(Y'_2 + Y'_1 + X'_2 + X_1)$$

$$\text{Dual} \rightarrow (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 Y_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (Y_1 + Y'_1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1 (1)) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y_1 X_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 X'_1) + (Y'_2 Y'_1 X'_2 X_1) + (Y'_2 Y'_1 X_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (Y'_2 X_2 X_1) + (Y'_2 Y'_1 X_2 (X'_1 + X_1)) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (X_2 X_1 Y'_2) + (Y'_2 Y'_1 X_2 (1)) + (Y'_2 Y'_1 X'_2 X_1)$$

$$= (Y_2 Y'_1 X_2 X_1) + (X_2 X_1 Y'_2) + (Y'_2 Y'_1 X_2) + (Y'_2 Y'_1 X'_2 X_1)$$

Are we done?! Honestly, I don't know ☹️ 😊

MINIMIZATION

I) Boolean Algebra (algebraically)

- Needs to be smart. It is hard due to guesswork (which rules to apply?)
- If the number of variables (ABCDEF...) and/or number of minterms (MAXTERMS) grows
- No Algorithm
- Is the result minimal?!

MINIMIZATION

II) Map (Karnaugh map, K-map)
aka. Graphical Manipulation

MINIMIZATION

II) Map (Karnaugh map, K-map) aka. Graphical Manipulation

Algorithm; Straightforward, up to six variables

Result is always minimal

MINIMIZATION

II) Map (Karnaugh map, K-map) aka. Graphical Manipulation

Algorithm; Straightforward, up to six variables


Result is always minimal

Maurice Karnaugh

Physicist
Mathematician
Inventor

Bell Labs (1954)

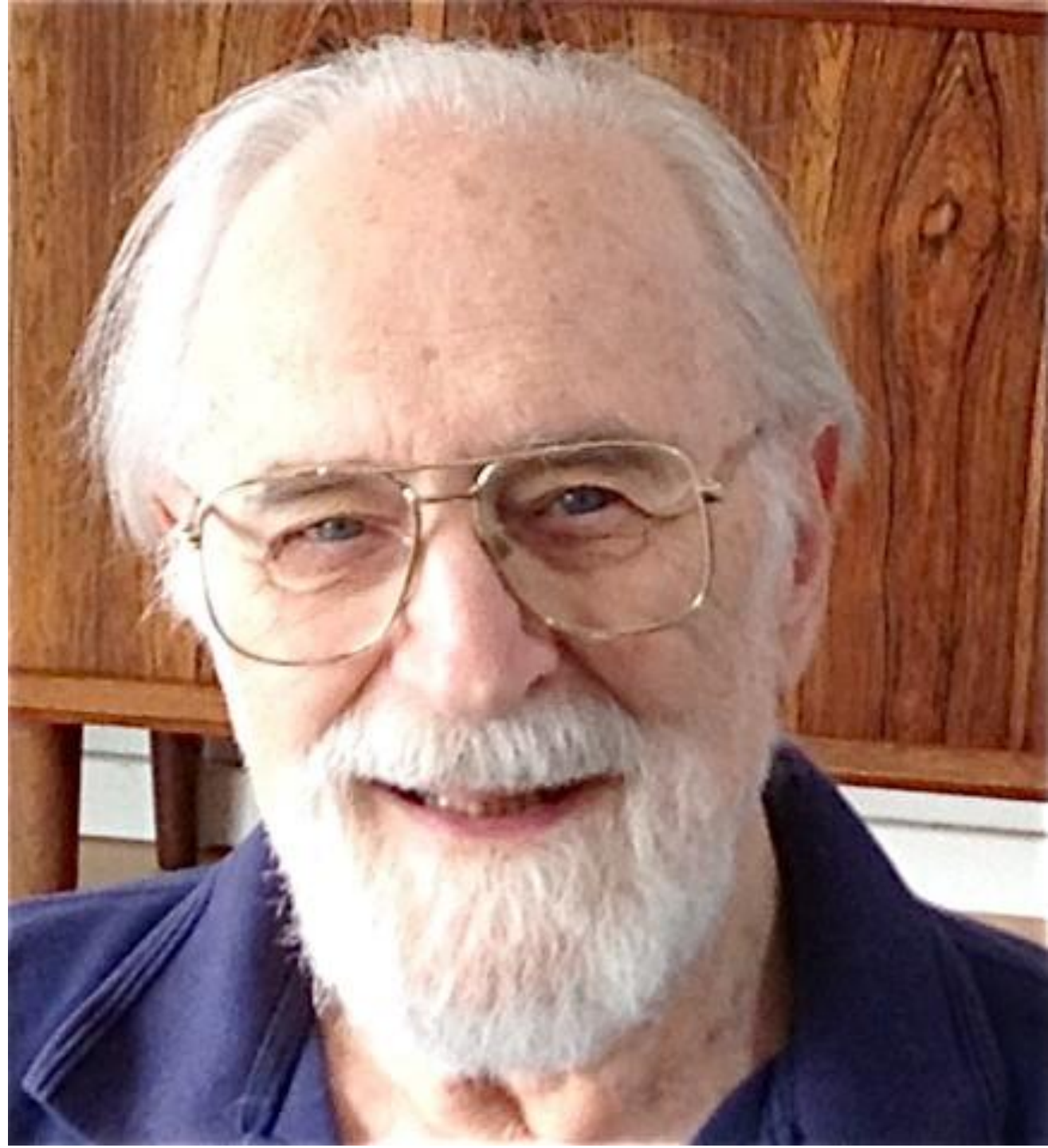"The Map Method for Synthesis of
Combinational Logic Circuits"



MINIMIZATION

II) Map (Karnaugh map, K-map)
aka. Graphical Manipulation

KARNAUGH MAP

/ˈkɑːrnɔː/

1-Variable KARNAUGH MAP

X	F
0	m_0
1	m_1


X	
0	1
m_0	m_1

2-Variable KARNAUGH MAP

Y	X	F
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3

Y	X	F
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

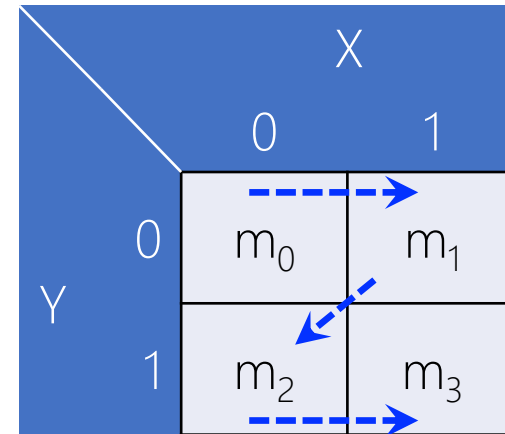

Y	X	F
0	0	1
0	1	0
1	0	0
1	1	0

$$F(Y,X) = m_0 = Y'X'$$

		X	
		0	1
Y	0	1	0
	1	0	0

$$F(Y,X) = Y'X'$$

Y	X	F
0	0	0
0	1	1
1	0	0
1	1	0

$$F(Y,X) = m_1 = Y'X$$

		X	
		0	1
Y	0	0	1
	1	0	0

$$F(Y,X) = Y'X$$

Y	X	F
0	0	0
0	1	0
1	0	1
1	1	0

$$F(Y,X) = m_2 = YX'$$

		X	
		0	1
Y	0	0	0
	1	1	0

$$F(Y,X) = YX'$$

Y	X	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F(Y,X) = m_3 = YX$$

		X	
		0	1
Y	0	0	0
	1	0	1

$$F(Y,X) = YX$$

Y	X	F
0	0	1
0	1	1
1	0	0
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 \\
 &= Y'X' + Y'X \\
 &= Y'(X' + X) \\
 &= Y'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	0	0

$$F(Y,X) = Y'$$

Y	X	F
0	0	0
0	1	0
1	0	1
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_2 + m_3 \\
 &= YX' + YX \\
 &= Y(X' + X) \\
 &= Y
 \end{aligned}$$

		X	
		0	1
Y	0	0	0
	1	1	1

$$F(Y,X) = \underline{Y}$$

Y	X	F
0	0	0
0	1	1
1	0	0
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_1 + m_3 \\
 &= Y'X + YX \\
 &= X(Y' + Y) \\
 &= X
 \end{aligned}$$

		X	
		0	1
Y	0	0	1
	1	0	1

$$F(Y,X) = X$$

Y	X	F
0	0	1
0	1	0
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_2 \\
 &= Y'X' + YX' \\
 &= X'(Y' + Y) \\
 &= X'
 \end{aligned}$$

		X	
		0	1
Y	0	1	0
	1	1	0

$$F(Y,X) = X'$$

WHAT IF

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= Y'(X' + X) + YX' \\
 &= Y' + YX'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = Y' + YX'$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= X'(Y' + Y) + Y'X \\
 &= X' + Y'X
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = X' + Y'X$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= Y'X' + Y'X' + Y'X + YX' \\
 &= Y'(X' + X) + Y'X' + YX' \\
 &= Y' + Y'X' + YX' \\
 &= Y' + X'(Y' + Y) \\
 &= Y' + X'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = Y' + X'$$

WHAT IF

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 + m_3 \\
 &= Y'X' + Y'X + YX' + YX \\
 &= Y'(X' + X) + Y(X' + X) \\
 &= Y' + Y \\
 &= 1
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 + m_3 \\
 &= 1
 \end{aligned}$$

Y	X	F
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_1 + m_2 \\
 &= Y'X + YX'
 \end{aligned}$$

		X	
		0	1
Y	0	0	1
	1	1	0

$$\begin{aligned}
 F(Y,X) &= m_1 + m_2 \\
 &= Y'X + YX'
 \end{aligned}$$

Y	X	F
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_3 \\
 &= Y'X' + YX
 \end{aligned}$$

		X	
		0	1
Y	0	1	0
	1	0	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_2 \\
 &= Y'X' + YX
 \end{aligned}$$

3-Variable KARNAUGH MAP

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7



		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3

		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3



		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

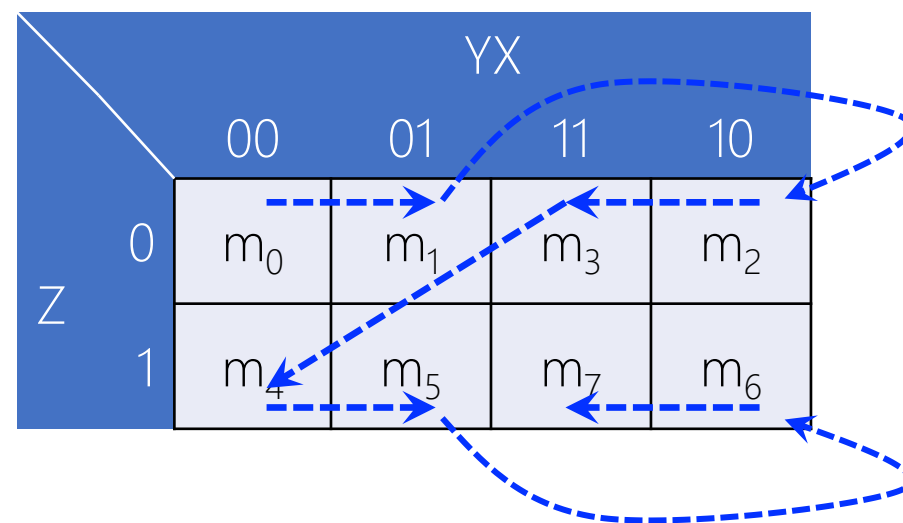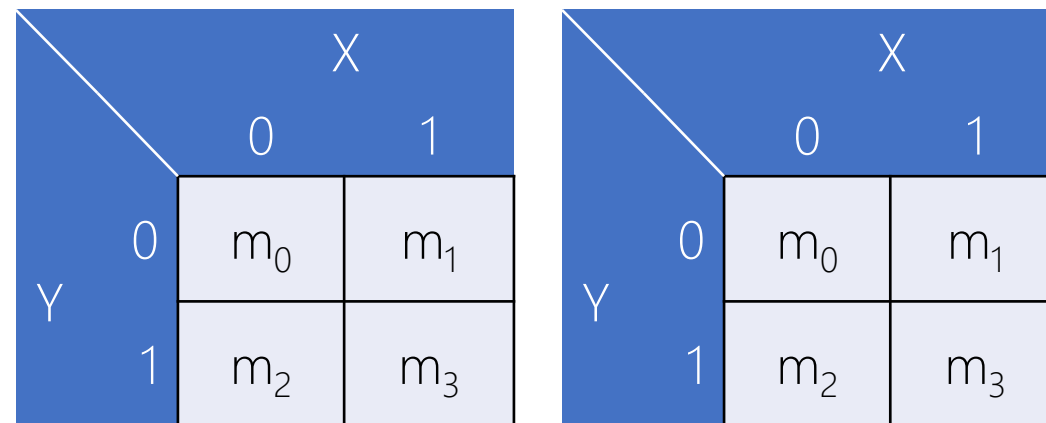

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

} Z

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

} Z'

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6



Y

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6



 Y'

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

X


Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

$X' ?$

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7


		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

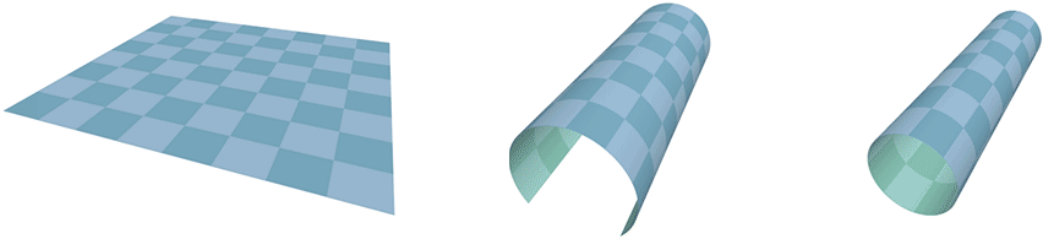

Click to Play!

https://en.wikipedia.org/wiki/Karnaugh_map#/media/File:Torus_from_rectangle.gif

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

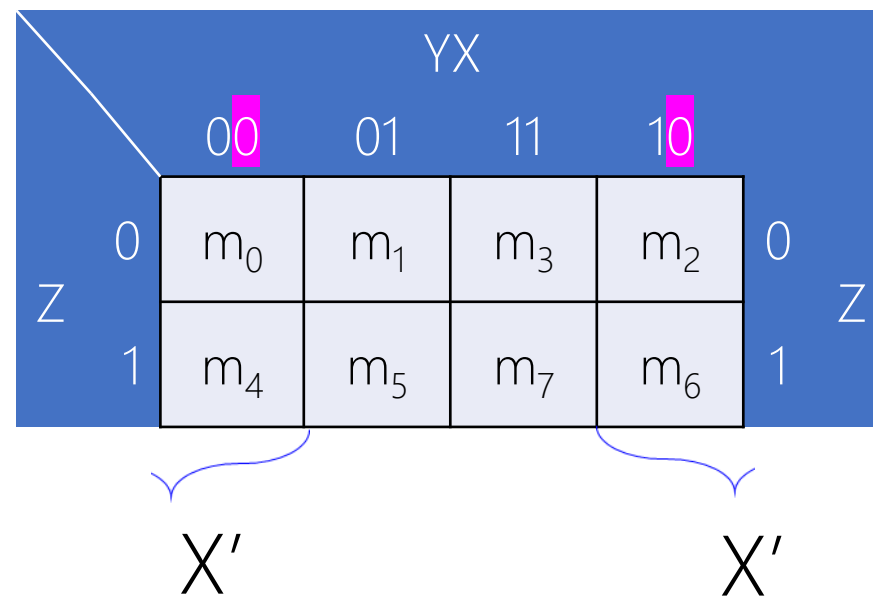

WHAT IF

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' +
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' + ZY
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$


$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' + Y
 \end{aligned}$$

WHAT IF

Z	Y	X	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,2,4, 6) \\
 &= Z'Y'X' + Z'YX' + ZY'X' + ZYX' \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	0	0	1
	1	1	0	0	1

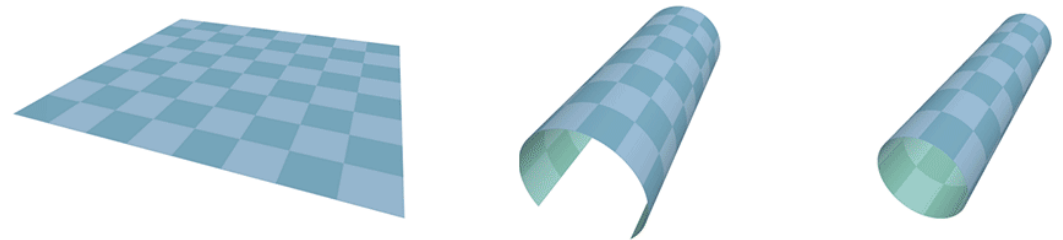

Z	Y	X	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,2,4, 6) \\
 &= Z'Y'X' + Z'YX' + ZY'X' + ZYX' \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	0	0	1
	1	1	0	0	1

$$\begin{aligned}
 F(Z,Y,X) &= \sum m(0,2,4, 6) \\
 &= X'
 \end{aligned}$$

4-Variable KARNAUGH MAP
