 
 
 
 

Flip-Flop

A single edge triggered latch




S	R	Q
0	0	Q_t
0	1	0
1	0	1
1	1	$\times$

D	Q
0	0
1	1

T	Q
0	Q_t
1	Q'_t


J	K	Q
0	0	Q_t
0	1	0
1	0	1
1	1	Q'_t

Single Edge *Positive*

 

Analysis: Given a sequential circuit, show the behavior
vs.

 Design: Given a behavior, build the sequential circuit



Analysis (Recap)

0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? $2^{\#FF}$
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: $2^{\#FF}$
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-

Design (Recap)



0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. Form the state (transition) diagram
 3. Form the state table
 4. Fill the state table
 5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 6. Input (*excitation*) equations for each FF
 7. Minimization of input (*excitation*) equations
 8. Draw/Sketch Logic Circuit
 9. (Optional) Test
-

Practice


Step Counter: Skip Every Other Number

$0 \rightarrow 2 \rightarrow 4 \rightarrow 6$

  $1 \rightarrow 3 \rightarrow 5 \rightarrow 7$



$Q(T)$			$Q(T+1)$			A	
C	B	A	C	B	A	Action	T_A
0	0	0	0	0	0	hold	0
0	0	1	0	1	1	hold	0
0	1	0	0	0	0	hold	0
0	1	1	1	0	1	hold	0
1	0	0	1	1	0	hold	0
1	0	1	1	1	1	hold	0
1	1	0	0	0	0	hold	0
1	1	1	0	0	1	hold	0

 

Action	R	S	C	K
set	0	1	0	X
	0	1	0	X
	1	0	1	X
	1	0	1	X
	0	1	X	0
	0	1	X	0
	1	0	X	1
	1	0	X	1


$$T_A = 0$$

$$R_B = \Sigma(2, 3, 6, 7) = B$$

$$S_B = \Sigma(0, 1, 4, 5) = B + B' = B$$

$$D_C = \Sigma(2, 3) + D(4-7) = B$$

$$K_C = \Sigma(6, 7) + D(0-3) = B$$

 

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. Form the state (transition) diagram
 3. Form the state table
 4. Fill the state table
 5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 6. Input (*excitation*) equations for each FF
 7. Minimization of input (*excitation*) equations
 8. Draw/Sketch Logic Circuit
 9. (Optional) Test
-

Design (Advanced)

0. Do we need combinational logic or sequential logic? Do we need memory?

1. How many storage (flip-flops)? #FF

2. Form the state (transition) diagram

2.1. State Reduction

3. Form the state table

4. Fill the state table

5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed

6. Input (*excitation*) equations for each FF


7. Minimization of input (*excitation*) equations

8. Draw/Sketch Logic Circuit

 
9. (Optional) Test


Theory of Automata

COMP-2140: Computer Languages, Grammars, and Translators



Analysis
vs.
Design

 

 

George H. Mealy

(1927 – 2010)

Mathematician and Computer Scientist

Invented Mealy Machine

Also a pioneer of modular programming

Outputs = Function(Current State, Inputs)


Edward Forrest Moore

(1925 – 2003)

Mathematician and Computer Scientist

Inventor of the Moore Machine

Also an early pioneer of artificial life

 

Outputs = Function(Current State, Inputs)


 


FIGURE 5.21
Block diagrams of Mealy and Moore state machines

 


 



FIGURE 5.21
Block diagrams of Mealy and Moore state machines

 

Sequential
Logic

Flip-Flop
+
Inputs
+
Outputs

Mealy Model

 


Analysis (Moore model in output) by an example


Analysis (Recap)


0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? $2^{\#FF}$
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: $2^{\#FF}$
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-

Analysis (+ Input + Moore Model Output)

 
0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? ~~$2^{\#FF}$~~
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: ~~$2^{\#FF}$~~
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-




 

 

#FFs + #Inputs = 2+1 $\rightarrow 2^3 = 8$ combinations

 [illegible]

 


Q(T)		Q(T+1) when X=0		Q(T+1) when X=1		Outputs
B	A	B	A	B	A	F
						Moore model: does not depend on X


Alternative State Table

Analysis (Recap)

 
0. Is the circuit sequential or combinational? Sequential
 1. What are the flip-flops? T, JK
 2. What are the state combinations? $2^{\#FF} \times 2^{\#inputs} = 2^{\#FF+\#inputs} = 2^3 = 8$
 3. Form "State" table:
 - a) Columns:
 - For each FF, two columns: one for current state, one for next state
 - For each input, one column
 - For each output, one column
 - b) Rows: See item 2
 4. Fill the state table for
 - a) next state columns
 - b) the output value
-




Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0			0
0	0	1			0
0	1	0	Moore Model Only depends on current state X is not involved!		0
0	1	1			1
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

 

Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0		A=0 $J_A = XB = 00 = 0$ $K_A = B' = 0' = 1$ ----- Reset $\rightarrow 0$	0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0

 


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	$F = BA$
0	0	0	B=0 $T_B = XA = 00 = 0$ ----- Store $\rightarrow 0$	0	0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0
1	0	1			0

 

Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	1	1


Analysis (Recap)

 0. Is the circuit sequential or combinational? Sequential
 1. What are the flip-flops? T, JK
 2. What are the state combinations? $2^{\#FF} \times 2^{\#inputs} = 2^{\#FF+\#inputs} = 2^3 = 8$
 3. Form "State" table:
 - a) Columns:
 - For each FF, two columns: one for current state, one for next state
 - For each input, one column
 - For each output, one column
 - b) Rows: See item 2
 4. Fill the state table for
 - a) next state columns
 - b) the output value
 5. Form state (transition) diagram
 - a) nodes for states, directed edges for transitions between states
 - b) labels for edges by the value of input
 - c) labels for nodes by the value of output
-





BA

Labels on edges
based on value of X

 


Labels on nodes
based on value of **F**

  

Analysis




6) (*Optional*) Path on State Transitions

Life lock!

 


Synchronization


Practice Timing Diagram

   

Asynchronized

 


Mealy Model
 F depends on X

 


Mealy Model

 
F depends on X , so, F can change out of Clk synchronization!



Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	$F = XBA$
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	1	1

Labels go on edges
for F:

 

 

Design by an example

Counter Up-Down

Switch to count up from i to $i+1$

Switch to count down from i to $i-1$

Turn **on** the light if the current number is **even**

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?

Counter up/down

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow \dots \rightarrow N-1 \rightarrow N$

$N \rightarrow N-1 \rightarrow \dots \rightarrow 3 \rightarrow 2 \rightarrow 1 \rightarrow 0$

Design (Recap)

- 0. Do we need combinational logic or sequential logic? Do we need memory?
- 1. How many storage (flip-flops)? #FF

Counter up/down N=7

000→001→010→011→100→101→110→111

000←001←010←011←100←101←110←111

For each intermediate state, we need 3 bits → 3 flip-flops

Design (Recap)

- 0. Do we need combinational logic or sequential logic? Do we need memory?
 - 1. How many storage (flip-flops)? #FF
 - 2. How many input and output?
-

Counter up/down

N=7

000→001→010→011→100→101→110→111

000←001←010←011←100←101←110←111

We need to switch between up and down → 1 binary variable

X=0 Count Up

X=1 Count Down

Counter up/down

N=7


X=0: 000 → 001 → 010 → 011 → 100 → 101 → 110 → 111


X=1: 111 → 110 → 101 → 100 → 011 → 010 → 001 → 000


We need to turn on the light when the number is even
→ 1 binary variable → F

Design (Recap)

 0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
-



 


 

F=1 : even

F=0 : else

Moore model

 

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
 4. Form the state table
 5. Fill the state table
-

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	F
0	0	0	0	0	0	1	
0	0	0	1	0	1	0	
0	0	1	0	0	1	1	
0	0	1	1	1	0	0	Count Up X=0
0	1	0	0	1	0	1	
0	1	0	1	1	1	0	
0	1	1	0	1	1	1	
0	1	1	1	0	0	0	
1	0	0	0	1	1	1	
1	0	0	1	0	0	0	
1	0	1	0	0	0	1	
1	0	1	1	0	1	0	Count Down X=1
1	1	0	0	0	1	1	
1	1	0	1	1	0	0	
1	1	1	0	1	0	1	
1	1	1	1	1	1	0	

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	F
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	1	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0

F depends only on
current state of
CBA

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	F
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	1	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0


Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
 4. Form the state table
 5. Fill the state table
 6. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
-

Counter Up/Down

Let's pick mix FFs: $1 \times T\text{-FF}$, $1 \times D\text{-FF}$, $1 \times JK\text{-FF}$

X —

 


— F

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
 4. Form the state table
 5. Fill the state table
 6. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 7. Input (*excitation*) equations for each FF
 8. Minimization of input (*excitation*) equations
-

Excitation Equations		
A	$J_A = F(\textcolor{red}{X}, C, B, A)$	$K_A = F(\textcolor{red}{X}, C, B, A)$
B	$D_B = F(\textcolor{red}{X}, C, B, A)$	
C	$T_C = F(\textcolor{red}{X}, C, B, A)$	

 

Excitation Equations

A	$J_A = F(X, C, B, A)$	$K_A = F(X, C, B, A)$
B	$D_B =$	
C	$T_C =$	

Inputs	Q(T)			Q(T+1)			Outputs	Excitation for A			
X	C	B	A		C	B	A	F	Action	J _A	K _A
0	0	0	0		0	0	1	1	Set/Cmp	1	×
0	0	0	1		0	1	0	0	Rst/Cmp	×	1
0	0	1	0		0	1	1	1	Set/Cmp	1	×
0	0	1	1		1	0	0	0	Rst/Cmp	×	1
0	1	0	0		1	0	1	1	Set/Cmp	1	×
0	1	0	1		1	1	0	0	Rst/Cmp	×	1
0	1	1	0		1	1	1	1	Set/Cmp	1	×
0	1	1	1		0	0	0	0	Rst/Cmp	×	1
1	0	0	0		1	1	1	1	Set/Cmp	1	×
1	0	0	1		0	0	0	0	Rst/Cmp	×	1
1	0	1	0		0	0	1	1	Set/Cmp	1	×
1	0	1	1		0	1	0	0	Rst/Cmp	×	1
1	1	0	0		0	1	1	1	Set/Cmp	1	×
1	1	0	1		1	0	0	0	Rst/Cmp	×	1
1	1	1	0		1	0	1	1	Set/Cmp	1	×
1	1	1	1		1	1	0	0	Rst/Cmp	×	1

Excitation Equations

A	$J_A = \sum(0,2,4,6,8,10,12,14) + d(1,3,5,7,9,11,13,15)$	$K_A = \sum(1,3,5,7,9,11,13,15) + d(0,2,4,6,8,10,12,14)$
B	$D_B =$	
C	$T_C =$	

Inputs	Q(T)				Q(T+1)			Outputs	Excitation for B		
X	C	B	A		C	B		A	F	Action	D _B
0	0	0	0		0	0		1	1	Rst	0
0	0	0	1		0	1		0	0	Set	1
0	0	1	0		0	1		1	1	Set	1
0	0	1	1		1	0		0	0	Rst	0
0	1	0	0		1	0		1	1	Rst	0
0	1	0	1		1	1		0	0	Set	1
0	1	1	0		1	1		1	1	Set	1
0	1	1	1		0	0		0	0	Rst	0
1	0	0	0		1	1		1	1	Set	1
1	0	0	1		0	0		0	0	Rst	0
1	0	1	0		0	0		1	1	Rst	0
1	0	1	1		0	1		0	0	Set	1
1	1	0	0		0	1		1	1	Set	1
1	1	0	1		1	0		0	0	Rst	0
1	1	1	0		1	0		1	1	Rst	0
1	1	1	1		1	1		0	0	Set	1

Excitation Equations

A	$J_A = \sum(0,2,4,6,8,10,12,14) + d(1,3,5,7,9,11,13,15)$	$K_A = \sum(1,3,5,7,9,11,13,15) + d(0,2,4,6,8,10,12,14)$
B	$D_B = \sum(1,2,5,6,8,11,12,15)$ <i>Never "don't care condition" happens in D-FF</i>	
C	$T_C =$	

Inputs	Q(T)			Q(T+1)			Outputs	Excitation for C	
X	C	B	A	C	B	A	F	Action	T _c
0	0	0	0	0	0	1	1	Store	0
0	0	0	1	0	1	0	0	Store	0
0	0	1	0	0	1	1	1	Store	0
0	0	1	1	1	0	0	0	Comp	1
0	1	0	0	1	0	1	1	Store	0
0	1	0	1	1	1	0	0	Store	0
0	1	1	0	1	1	1	1	Store	0
0	1	1	1	0	0	0	0	Comp	1
1	0	0	0	1	1	1	1	Comp	1
1	0	0	1	0	0	0	0	Store	0
1	0	1	0	0	0	1	1	Store	0
1	0	1	1	0	1	0	0	Store	0
1	1	0	0	0	1	1	1	Comp	1
1	1	0	1	1	0	0	0	Store	0
1	1	1	0	1	0	1	1	Store	0
1	1	1	1	1	1	0	0	Store	0

Excitation Equations

A	$J_A = \sum(0,2,4,6,8,10,12,14) + d(1,3,5,7,9,11,13,15)$	$K_A = \sum(1,3,5,7,9,11,13,15) + d(0,2,4,6,8,10,12,14)$
B	$D_B = \sum(1,2,5,6,8,11,12,15)$ <i>Never "don't care condition" happens in D-FF</i>	
C	$T_C = \sum(3,7,8,12)$ <i>Never "don't care condition" happens in T-FF</i>	

Minimization for excitation equations

?-Variable K-Map

Excitation Equations		
A	$J_A = \sum(0,2,4,6,8,10,12,14) + d(1,3,5,7,9,11,13,15)$	$K_A = \sum(1,3,5,7,9,11,13,15) + d(0,2,4,6,8,10,12,14)$
B	$D_B = \sum(1,2,5,6,8,11,12,15)$ Never "don't care condition" happens in D-FF	
C	$T_C = \sum(3,7,8,12)$ Never "don't care condition" happens in T-FF	

Minimization
 4-Variable K-Map
 $F(\textcolor{red}{X}, C, B, A)$

		BA			
		00	01	11	10
XC	00	0 m_0	0 m_1	1 m_3	0 m_2
	01	0 m_4	0 m_5	1 m_7	0 m_6
	11	1 m_{12}	0 m_{13}	0 m_{15}	0 m_{14}
	10	1 m_8	0 m_9	0 m_{11}	0 m_{10}

$$T_C = \sum(3, 7, 8, 12) \\ = X'BA + XB'A'$$

		BA			
		00	01	11	10
XC	00	0 m_0	1 m_1	0 m_3	1 m_2
	01	0 m_4	1 m_5	0 m_7	1 m_6
	11	1 m_{12}	0 m_{13}	1 m_{15}	0 m_{14}
	10	1 m_8	0 m_9	1 m_{11}	0 m_{10}

$$D_B = \sum(1, 2, 5, 6, 8, 11, 12, 15) \\ = X'B'A + X'BA' + XB'A' + XBA \\ = X'(B'A + BA') + X(B'A' + BA) \\ = X'(B \oplus A) + X(B \odot A) \\ = X \oplus B \oplus A$$

		BA			
		00	01	11	10
XC	00	1 m_0	X m_1	X m_3	1 m_2
	01	1 m_4	X m_5	X m_7	1 m_6
	11	1 m_{12}	X m_{13}	X m_{15}	1 m_{14}
	10	1 m_8	X m_9	X m_{11}	1 m_{10}

$$J_A = \sum(0, 2, 4, 6, 8, 10, 12, 14) + \\ d(1, 3, 5, 7, 9, 11, 13, 15) = 1$$

		BA			
		00	01	11	10
XC	00	X m_0	1 m_1	1 m_3	X m_2
	01	X m_4	1 m_5	1 m_7	X m_6
	11	X m_{12}	1 m_{13}	1 m_{15}	X m_{14}
	10	X m_8	1 m_9	1 m_{11}	X m_{10}

$$K_A = \sum(1, 3, 5, 7, 9, 11, 13, 15) + \\ d(0, 2, 4, 6, 8, 10, 12, 14) = 1$$

Excitation Equations

A	$J_A = 1$	$K_A = 1$
B	$D_B = F(X, C, B, A) = X \oplus B \oplus A$	
C	$T_C = F(X, C, B, A) = X'BA + XB'A'$	

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
 4. Form the state table
 5. Fill the state table
 6. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 7. Input (*excitation*) equations for each FF
 8. Minimization of input (*excitation*) equations
 9. Boolean function for the output
 10. Minimization of output variable
-

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	F
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	1	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	Y
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	1	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0

$$F = F(C,B,A) = \sum(0,2,4,6)$$

Inputs	Q(T)			Q(T+1)			Outputs
X	C	B	A	C	B	A	Y
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	1
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	1	0	0
0	1	1	0	0	1	1	1
0	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	1	1
1	1	0	1	1	0	0	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0

~~Incorrect but if we make a mistake that X is involved:~~
 ~~$F = F(X, C, B, A) = \sum(0, 2, 4, 6, 8, 10, 12, 14)$~~

Minimization for output Y

3-Variable K-Map

~~Incorrectly 4-Variable K-Map~~

		BA			
		00	01	11	10
C	0	1 m_0	0 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	0 m_7	1 m_6

$$F = F(C,B,A) = \sum(0,2,4,6) \\ = A'$$

Even if we consider the input, because Y does not depend on X in the state table, it will disappear in simplification!


		BA			
		00	01	11	10
XC	00	1 m_0	0 m_1	0 m_3	1 m_2
	01	1 m_4	0 m_5	0 m_7	1 m_6
	11	1 m_{12}	0 m_{13}	0 m_{15}	1 m_{14}
	10	1 m_8	0 m_9	0 m_{11}	1 m_{10}

$$F = F(X,C,B,A) = \sum(0,2,4,6,8,10,12,14) \\ = A'$$


Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. How many input and output?
 3. Form the state (transition) diagram
 4. Form the state table
 5. Fill the state table
 6. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 7. Input (*excitation*) equations for each FF
 8. Minimization of input (*excitation*) equations
 9. Boolean function for the output
 10. Minimization of output variable
 11. Draw/Sketch Logic Circuit
 12. (Optional) Test
-


X —

 


A	$J_A = 1$	$K_A = 1$
B	$D_B = F(X, C, B, A) = X \oplus B \oplus A$	
C	$T_C = F(X, C, B, A) = X'BA + XB'A'$	
F	$F(C, B, A) = A'$	

 

A	$J_A = 1$	$K_A = 1$
B	$D_B = F(X, C, B, A) = X \oplus B \oplus A$	
C	$T_C = F(X, C, B, A) = X'BA + XB'A'$	
F	$F(C, B, A) = A'$	

 


A	$J_A = 1$	$K_A = 1$
B	$D_B = F(X, C, B, A) = X \oplus B \oplus A$	
C	$T_C = F(X, C, B, A) = X'BA + XB'A'$	
F	$F(C, B, A) = A'$	

 

A	$J_A = 1$	$K_A = 1$
B	$D_B = F(X, C, B, A) = X \oplus B \oplus A$	
C	$T_C = F(X, C, B, A) = X'BA + XB'A'$	
F	$F(C, B, A) = A'$	

Synchronization

Practice Timing Diagram

 

2001: A Space Odyssey (Stanley Kubrick-1968)

Number Systems |

| Computer Systems

Number Systems | $(12)_{10} \rightarrow (1100)_2$


| Computer Systems

Number Systems | $(12)_{10} \rightarrow (1100)_2$
| Logic Gates | 

| Computer Systems

Number Systems | $(12)_{10} \rightarrow (1100)_2$


| Logic Gates | 
 
| Combinational Logic | 


| Computer Systems

Number Systems | $(12)_{10} \rightarrow (1100)_2$

| Logic Gates | 
 
| Combinational Logic | 


| Flip-Flops |

 


| Computer Systems

Number Systems | $(12)_{10} \rightarrow (1100)_2$


| Logic Gates | 
 
| Combinational Logic | 

| Flip-Flops |

 

| Sequential Logic |

 

| Computer Systems

Design a Computer System

John von Neumann

([/vɒn ˈnɔɪmən/](#))

1903 –1957


Mathematician, Physicist, Computer Scientist, Engineer

Polymath

He integrated pure and applied sciences. He made major contributions to many fields, including:

 - Mathematics
- Physics
- Economics (game theory)
- Computing
- Statistics






von Neumann Architecture

Principles

- Data and instructions are both stored in the main memory
- The content of the memory is addressable by location (regardless of what is stored in that location)
- Instructions are executed sequentially unless the order is explicitly modified

Human Natural Language	Type	Example
High Level Programing Language	Imperative (What)	SQL <code>SELECT * FROM Students</code>
Middle Level Programming Language	Declarative (What + How)	C, C++, Java, Python <code>int a = 1;</code> <code>a = a + 1;</code>
Low Level Programming Language (Assembly Language)		Assembly x86, Assembly Z80 <code>MOV 1, AX</code> <code>INC AX</code>
Binary Digits (Machine Language)		<code>00010011</code> <code>00001011</code>

Human Natural Language		Example
High Level Programing Language	Impera	SQL <code>SELECT * FROM Students</code>
Middle Level Programming Language	Declar (how)	C, C++, Java, Python <code>int a = 1; a = a + 1;</code>
Low Level Programming Language (Assembly Language)		Assembly x86, Assembly Z80 <code>MOV 1, AX INC AX</code>
Binary Digits (Machine Language)		<code>00010011 00001011</code>

 

Compilers
Interpreters

C/C++

Hossein's Computer

Debug COMP2650_W13_hfani.exe

COMP2650_W13_hfani.c

main() at COMP2650_W13_hfani.c:2 0x10040108d

COMP2650_W13_hfani.exe [C/C++ Application]

COMP2650_W13_hfani.exe [13164]

Thread #1 [COMP2650_W13_hfani] 0 (Suspended)

main() at COMP2650_W13_hfani.c:2 0x10040108d

Thread #2 0 (Suspended: Container)

Thread #3 0 (Suspended: Container)

Thread #4 [sig] 0 (Suspended: Container)

gdb (8.3.1)

```
1 int main(void) {
2     int a=1;
3     int b=2;
4     int c;
5     c = a + b;
6
7     return 0;
8 }
9
```

0000000010040107e: nop
0000000010040107f: nop
main:
00000000100401080: push %rbp
00000000100401081: mov %rsp,%rbp
00000000100401084: sub \$0x30,%rsp
00000000100401088: callq 0x1004010d0 <__main>
0000000010040108d: movl \$0x1,-0x4(%rbp)
00000000100401094: movl \$0x2,-0x8(%rbp)
0000000010040109b: mov -0x4(%rbp),%edx
0000000010040109e: mov -0x8(%rbp),%eax
000000001004010a1: add %edx,%eax
000000001004010a3: mov %eax,-0xc(%rbp)
000000001004010a6: mov \$0x0,%eax
000000001004010ab: add \$0x30,%rsp
000000001004010af: pop %rbp
000000001004010b0: retq
000000001004010b1: nop
000000001004010b2: nop
000000001004010b3: nop

Console Registers Problems Executables Debugger Console Memory

COMP2650_W13_hfani.exe [C/C++ Application]

Writable Smart Insert 3 : 1 [10]

Debug COMP2650_W13_hfani.exe

Project Explorer

- COMP2650_W13_hfani.exe [C/C++ Application]
 - COMP2650_W13_hfani.exe [13164]
 - Thread #1 [COMP2650_W13_hfani] 0 (Suspended: Container)
 - main() at COMP2650_W13_hfani.c:2 0x10040108d
 - Thread #2 0 (Suspended: Container)
 - Thread #3 0 (Suspended: Container)
 - Thread #4 [sig] 0 (Suspended: Container)

gdb (8.3.1)

```
1 int main(void) {  
2     int a=1;  
3     int b=2;  
4     int c;  
5     c = a + b;  
6  
7     return 0;  
8 }  
9
```

main() at COMP2650_W13_hfani.c:2 0x10040108d

0000000010040107e: nop
0000000010040107f: nop
main:
00000000100401080: push %rbp
00000000100401081: mov %rsp,%rbp
00000000100401084: sub \$0x30,%rsp
00000000100401088: callq 0x1004010d0 <__main>
0000000010040108d: movl \$0x1,-0x4(%rbp)
00000000100401094: movl \$0x2,-0x8(%rbp)
0000000010040109b: mov -0x4(%rbp),%edx
0000000010040109e: mov -0x8(%rbp),%eax
000000001004010a1: add %edx,%eax
000000001004010a3: mov %eax,-0xc(%rbp)
000000001004010a6: mov \$0x0,%eax
000000001004010ab: add \$0x30,%rsp
000000001004010af: pop %rbp
000000001004010b0: retq
000000001004010b1: nop
000000001004010b2: nop
000000001004010b3: nop

Console COMP2650_W13_hfani.exe [C/C++ Application]

Writable Smart Insert 3 : 1 [10]

eclipse-workspace - COMP2650_W13_hfani/src/COMP2650_W13_hfani.c - Eclipse IDE

File Edit Source Refactor Navigate Search Project Run Window Help

Debug COMP2650_W13_hfani.exe

Project Explorer

- COMP2650_W13_hfani.exe [C/C++ Application]
- COMP2650_W13_hfani.exe [13164]
- Thread #1 [COMP2650_W13_hfani] 0 (Suspended)
- main() at COMP2650_W13_hfani.c:2 0x10040108d
- Thread #2 0 (Suspended: Container)
- Thread #3 0 (Suspended: Container)
- Thread #4 [sig] 0 (Suspended: Container)
- gdb (8.3.1)

```
1 int main(void) {  
2     int a=1;  
3     int b=2;  
4     int c;  
5     c = a + b;  
6  
7     return 0;  
8 }  
9
```

main() at COMP2650_W13_hfani.c:2 0x10040108d

0000000010040107e: nop
0000000010040107f: nop
main:
00000000100401080: push %rbp
00000000100401081: mov %rsp,%rbp
00000000100401084: sub \$0x30,%rsp
00000000100401088: callq 0x1004010d0 <__main>
0000000010040108d: movl \$0x1,-0x4(%rbp)
00000000100401094: movl \$0x2,-0x8(%rbp)
0000000010040109b: mov -0x4(%rbp),%edx
0000000010040109e: mov -0x8(%rbp),%eax
000000001004010a1: add %edx,%eax
000000001004010a3: mov %eax,-0xc(%rbp)
000000001004010a6: mov \$0x0,%eax
000000001004010ab: add \$0x30,%rsp
000000001004010af: pop %rbp
000000001004010b0: retq
000000001004010b1: nop
000000001004010b2: nop
000000001004010b3: nop

Memory Addresses

To see the actual binary machine language (OP Code) for each instruction, open your executable file that the compiler makes. E.g., *.exe in Windows systems.

ULNULNULNULNUL@NUL@B/70NULNULNULNULNULÂETXNULNULNULÐSTXNULNULEOTNULNULNUL.STXNULNUL

LEB/81NULNULNULNULNULBELNULNULNULàSTXNULNULBSNULNULNUL2STXNULNULNULNULNULNULNULNUL

[illegible][illegible][illegible][illegible][illegible][illegible][illegible][illegible][illegible][illegible][illegible][illegible]

ULNULNULNULNULNULNULNULNULNULNULNULNULNULNULNULNULHfì(H

E1À1Ò1Éè" NULNULNULE1À1Ò1Éè- NULNULNULE1À1Ò1ÉHfÄ(é- NULNULNULLENQ©SINULNUL1ÒH

ULNULNULNULÃÿ%.pNULNULÿ%&pNULNULHfì (lòèUNULNULNULÿNAKDC3pNULNULÃÃÃÃVSHfì (H%ÎH%Ó¹BSNUL

NULNULNULNULTSOHNULNULH%.s@H5EÿÿÿH

1%SPH<NAKxONULNULH%³€NULNULNULH5nÿÿH%KHH

$\ddot{y}\ddot{y}H^0<NULNULNULH^1H[SOHNULNUL^1VTNULNULH^0-3NULNULNULH^5[EOTNULNULH^0S8HNAK@EOTNULNULH^0KB$

$$\left[\text{CC}(\text{DLEBEL})\text{H} \cdot \text{KOH} \cdot s \cdot x \cdot \text{H} \right] \text{CAN SOHN} \text{H} \dots \text{SI} \cdot \frac{1}{2} \text{H} < \epsilon \text{a} \text{H} \dots \text{SI} \cdot -$$

HF=ETXSONULNULNULSI,,

MIT EVOC

Instruction	Operation Code (OP Code)
$c = a + b$	000 XXXX YYYY ZZZZ
$c = a - b$	001 XXXX YYYY ZZZZ
$c = a / b$	010 XXXX YYYY ZZZZ
$c = a * b$	011 XXXX YYYY ZZZZ
$c = \{\text{number}\}$	100 XXXX XXX XXXX
...	...

Instruction Encoders
very simplified version!

Design Processor

Processor can only see binary-coded instructions

Processor only understand machine language


Instruction Set → Instruction Decoder

Operation Code (OP Code)	What to do?
000 XXXX YYYY ZZZZ	1) Fetch the first operand from memory at XXXX address 2) Store the first operand inside somewhere (AX) 3) Fetch the second operand from memory at YYYY address 4) Store the first operand inside somewhere else (BX) 5) Use the n-bit Adder to add AX and BX 6) Store the result inside somewhere else (CX) 7) Push CX to memory at ZZZZ address
001 XXXX YYYY ZZZZ	
010 XXXX YYYY ZZZZ	
011 XXXX YYYY ZZZZ	
100 XXXX XXX XXXX	
...	

Instruction Decoder
very simplified version!

Operation Code (OP Code)	What to do?
000 XXXX YYYY ZZZZ	1) Fetch the first operand from memory at XXXX address 2) Store the first operand inside somewhere (AX) 3) Fetch the second operand from memory at YYYY address 4) Store the first operand inside somewhere else (BX) 5) Use the n-bit Adder to add AX and BX 6) Store the result inside somewhere else (CX) 7) Push CX to memory at ZZZZ address
001 XXXX YYYY ZZZZ	
010 XXXX YYYY ZZZZ	
011 XXXX YYYY ZZZZ	
100 XXXX XXX XXXX	
...	

 Instruction Decoder
very simplified version!





COMP-2660
Computer Architecture II
Microprocessor Programming



Starchild: **qbit**